

Digital Design with the Verilog HDL

Chapter 4 RTL Model

Binh Tran-Thanh

May 26, 2023

- Higher-level of description than structural
 - Don't always need to specify each individual gate
 - Can take advantage of **operators**
- More hardware-explicit than behavioral
 - Doesn't look as much like software
 - Frequently easier to understand what's happening
- Very easy to synthesize
 - Supported by even primitive synthesizers

Continuous Assignment

- Implies structural hardware

```
assign <LHS> = <RHS expression>;
```

- Example


```
wire out, a, b;  
assign out = a & b;
```

- If RHS result changes, LHS is updated with new value
 - Constantly operating (“continuous”!)
 - It’s **hardware!**
- Used to model combinational logic and latches


Full Adder: RTL/Dataflow

Example from Lecture 02

```
module fa_rtl (A, B, CI, S, CO);  
  input A, B, CI;  
  output S, CO;  
  
  // use continuous assignments  
  assign S = A ^ B ^ CI;  
  assign CO = (A & B) | (A & CI)  
             | (B & CI);  
endmodule
```

 

RTL And Structural Combined

 

```
module Add_half(sum,  
    cout, a, b);  
    output sum, cout;  
    input a, b;  
  
    assign sum = a ^ b;  
    assign cout = a & b;  
endmodule
```

```
module Add_full(c_out, sum, a, b,  
    c_in);  
    output sum, c_out;  
    input a, b, c_in;  
    wire psum, c1, c2;  
  
    Add_half AH1(partsum, c1, a, b);  
    Add_half AH2(sum, c2, psum, c_in);  
    assign c_out = c1 | c2;  
endmodule
```

Continuous Assignment LHS

Can assign values to

- Scalar nets
- Vector nets
- Single bits of vector nets
- Part-selects of vector nets
- Concatenation of any of the above

Examples

```
assign out[7:4] = a[3:0] | b[7:4];
```

```
assign val[3] = c & d;
```

```
assign {a, b} = stimulus[15:0];
```

```
____
```

Continuous Assignment RHS

Use operators

- Arithmetic, Logical, Relational, Equality, Bitwise, Reduction, Shift, Concatenation, Replication, Conditional
- Same set as used in Behavioral Verilog

Can also be a pass-through!

```
assign a = stimulus[16:9];  
assign b = stimulus[8:1];  
assign cin = stimulus[0];
```

- Note: “aliasing” is only in one direction
 - Cannot give ‘a’ a new value elsewhere to set stimulus[16:9]!

Implicit Continuous Assignments

- Can create an implicit continuous assign
- Goes in the wire declaration
`wire [3:0] sum = a + b;`
- Can be a useful shortcut to make code succinct, but doesn't allow fancy LHS combos
`assign {cout, sum} = a + b + cin;`
- Personal choice
 - You are welcome to use it when appropriate

Implicit Wire Declaration

- Can create an implicit wire
- When wire is used but not declared, it is implied

```
module majority(output out, input a, b, c);  
    assign part1 = a & b;  
    assign part2 = a & c;  
    assign part3 = b & c;  
    assign out = part1 | part2 | part3;  
endmodule
```

- Lazy! Don't do it!
 - Use explicit declarations
 - To design well, need to be "in tune" with design!

Verilog Operators

Operator	Name	Group	Example	Precedence
[]	Select		b[2:1] b[2]	
{}	Concatenation	Concat.	{a,b}	
{{} }	Replication	Repl.	{3{a}}	
!	Negation (inverse)	Logical	!a	1 (unary)
~	Negation (not)	Bit-wise	~ a	
&	Reduction AND	Reduction	& a	
	Reduction OR		a	
~ &	Reduction NAND		~ & a	
~	Reduction NOR		~ a	
^	Reduction XOR		^ a	
~ ^ or ^ ~	Reduction XNOR	~ ^ a		
+	Positive (unary)	Arithmetic	+ a	
-	Negative (unary)		- a	

Verilog Operators


Operator	Name	Group	Example	Precedence
* / %	Multiplication Division Modulus	Arithmetic	$a * b$ a / b $a \% b$	2 (binary)
+ -	Addition Subtraction		$a + b$ $a - b$	3 (binary)
<< >>	Shift left Shift right	Shift	$a << 4$ $a >> 4$	4 (binary)
> >= < >=	Greater Greater or equal Less Less or equal	Relational	$a > b$ $a >= b$ $a < b$ $a >= b$	5 (binary)

Verilog Operators

Operator	Name	Group	Example	Precedence
<code>==</code> <code>!=</code> <code>===</code> <code>!==</code>	Equal (logic) Not equal (logic) Equal (case) Not equal (case)	Equal	<code>a == b</code> <code>a != b</code> <code>a === b</code> <code>a !== b</code>	6 (binary)
<code>&</code> <code>^</code> <code>~ ^ or ^ ~</code> <code> </code>	bit-wise AND bit-wise XOR bit-wise XNOR bit-wise OR	Bit-wise	<code>a & b</code> <code>a ^ b</code> <code>a ~ ^ b</code> <code>a b</code>	7 (binary)
<code>&&</code> <code> </code>	logical AND logical OR	Logic	<code>a && b</code> <code>a b</code>	8 (binary)
<code>?:</code>	Conditional	Conditional	<code>a ? b : c</code>	9 (binary)


Arithmetic Operators (+, -, *, /, %)

 If any bit in the operands is **x** or **z**, the result will be **x**







The result's size

 - **Mul:** sum of both operands
- **Others:** size of the bigger operand



Relational Operators (<, >, <=, >=)

    

Equality Operators (==, ==~, !=, !~~~)

- Logical comparison (== and !=)
 - The **x** and **z** values are processed as in Relative operators
 - **The result may be x**
- Case comparison (~~~ and !~~~)
 - Bitwise compare
 - $x \text{ ~~~ } x, z \text{ ~~~ } z, x \text{ !~~~ } z$
 - **The result is always 0 or 1**
- If two operands are not the same size, **0(s)** will be inserted into **MSB** bits of the smaller operand

```
__Data = 4'b11x0;  
__Addr = 4'b11x0;  
__Data == Addr //x  
__Data ~~~ Addr //1
```

Logical Operators (||, &&, !)

- **Vector with at least one bit 1 is 1**
- **If any bit in the operands is x or z, the result will be x**

```
ABus = 4'b0110;  
BBus = 4'b0100;  
ABus || BBus // 1  
ABus && BBus // 1  
!ABus      // Similar to !BBus  
           // 0
```


Bit-wise Operators (&, |, ~, ^, ^ ~)

& (and)	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

 (or)	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x



^ (xor)	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

^ ~ (xnor)	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x



~ (not)	0	1	x	z
	1	0	x	x

Reduction Operators

Dont care (X) and HighZ (Z)

  


  &(and reduction): $\&b_n b_{n-1} \dots b_1 b_0$





Reduction Operators

 \sim & (nand reduction): $\sim \& b_n b_{n-1} \dots b_1 b_0$




| (or reduction): $| b_n b_{n-1} \dots b_1 b_0$

  

Reduction Operators

\sim | (or reduction): $\sim | b_n b_{n-1} \dots b_1 b_0$

 

\wedge (xor reduction): $\wedge b_n b_{n-1} \dots b_1 b_0$

If count $(b_i = 1) \bmod 2 == 0$ then return 0;


Otherwise return 1

$\sim \wedge / \wedge \sim$ (xnor reduction): $\sim \wedge b_n b_{n-1} \dots b_1 b_0$

Shift Operators (<<, >>)


Shift the left operand the number of times represented by the right operand

Shift left

 


```
reg [0:7] Qreg;  
Qreg = 4'b0111;  
    // 8'b0000_0111  
Qreg >> 2;  
    // 8'b0000_0001  
Qreg = 4'd1 << 5;  
    // 8'b0010_0000
```

Shift right

 

Conditional Operator `Cond_expr ? Expr1 : Expr2`

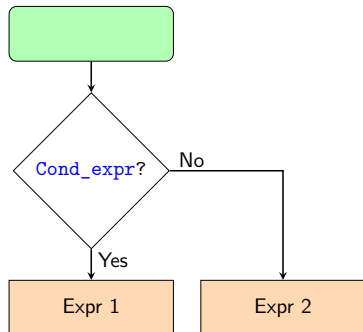- If `Cond_expr` includes any `x` bit or `z` bit, the result will be a “bitwise operation” of `Expr1` and `Expr2` as following:
 - `0 ♣ 0 ⇒ 0`
 - `1 ♣ 1 ⇒ 1`
 - otherwise `x`
- Infinite nested conditional operator



```
wire[15:0] bus_a = drive_a ? data : 16'bz;
```

```
__/* drive_a = 1 data is copied to bus_a
```

```
__ * drive_a = 0 bus_a is high-Z
```

```
__ * drive_a = x bus_a is x
```

```
__ */__
```

```
__
```

Concatenation and Replication Operators

- Concatenation {`expr1`, `expr2`, ... ,`exprN`}
 - Does not work with **un-sized constants**

```
wire [7:0] Dbus;  
wire [11:0] Abus;  
assign Dbus[7:4] = {Dbus[0],Dbus[1],Dbus[2],Dbus[3]};  
assign Dbus = {Dbus[3:0], Dbus[7:4]};  
//{Dbus, 5} // not allowed
```

- Replication {`rep_number`{`expr1`, `expr2`, ... , `exprN`}


```
Abus = {3{4'b1011}}; // 12'b1011_1011_1011  
{3{1'b1}} // 111  
{3{Ack}} // {Ack, Ack, Ack}
```

Expression Bit Lengths

Expression	Bit length	Comments
Unsigned constant number	Same as integer (32 bit)	
Sized constant number	As given	
$a <op> b$, where $<op>$ is: $+, -, *, /, \%, , \wedge, \sim \wedge$	$\text{Max}(L(a), L(b))$	$L(a)$: length (a)
$a <op> b$, where $<op>$ is: $==, !=, ==, !=, \&\&, , >, >=, <, <=$	1 bit	Operands are sized to $\text{Max}(L(i), L(j))$
$a <op> b$, where $<op>$ is: $\&, \sim \&, , \sim , \wedge, \sim \wedge, !$	1 bit	
$a <op> b$, where $<op>$ is: $>>, <<$	$L(i)$	

 Example: adder4b

```
module adder4b (sum, c_out, a, b, c_in);  
    input [3:0] a, b;  
    input c_in;  
    output [3:0] sum;  
    output c_out;  
  
    assign {c_out, sum} = a + b + c_in;  
  
endmodule
```



Example: Unsigned MAC Unit

Design a multiply-accumulate (MAC) unit that computes

$$Z[7:0] = A[3:0]*B[3:0] + C[7:0]$$

It sets overflow to one, if the result cannot be represented using 8 bits.

```
module mac(output [7:0] Z, output overflow,  
           input [3:0] A, B, input [7:0] C);  
    _____
```

Solution: Unsigned MAC Unit

```
module mac(output [7:0] Z, output overflow,  
           input[3:0] A, B, input[7:0] C);  
  wire [8:0] P;  
  assign P = A*B + C;  
  assign Z = P[7:0];  
  assign overflow = P[8];  
endmodule
```

Alternative method:

```
module mac(output[7:0] Z, output overflow,  
           input[3:0] A, B, input[7:0] C);  
  assign {overflow, Z} = A*B + C;  
endmodule
```


Example: Multiplexer

Use the conditional operator and a single continuous assignment statement

```
module mux_8_to_1(output out,  
    input in0, in1, in2, in3, in4, in5, in6, in7,  
    input [2:0] sel);
```

```
endmodule
```

Latches

 

Latches

- Continuous assignments with feedback

```
module latch(output [7:0] q_out,  
             input [7:0] data_in, enable);  
    assign q_out = enable ? data_in: q_out;  
endmodule
```

```
module latch_reset(output q_out,  
                  input data_in, enable, reset);  
    assign q_out = reset ? 0 : (enable ? data_in: q_out);  
endmodule
```

- How would we change these for 8-bit latches?
- How would we make the enable active low?

Example: Rock-Paper-Scissors (optional homework)

- `module rps(win, player, p0guess, p1guess);`
- Assumptions:
 - Input: p0guess, p1guess = 0 for rock, 1 for paper, 2 for scissors
 - Output: player is 0 if p0 wins, 1 if p1 wins, and don't care if there is a tie
 - Output: win is 0 if there is a tie and 1 if a player wins
- Reminders
 - Paper beats rock, scissors beats paper, rock beats scissors
 - Same values tie
- Two possible approaches
 - Figure out the Boolean equations for win and player and implement these using continuous assignments
 - Use bitwise operators
 - Examine what the various items equal and do logical operations on these
 - Use equality and logical operators

Draw synthesized hardware of following verilogHDL

```
wire [3:0] a, b, c;  
wire [7:0] d;  
assign c = d[7:4] + b;  
assign d = a * b;  
_____
```

```
wire [3:0] a, b, c;  
assign c = !a && b ? a + b : a - b;  
_____
```


Take away message

- Using continuous assign: `assign LHS = RHS.`
- Operation and its order.
- Length of inputs, output.